

Some of the Big Ideas in Electronics

Joseph Cunningham

Contents

0	Preface	9
I	Introducing some basic ideas	10
1	Different types of circuits	12
1.1	Basic circuits	12
1.1.1	Wires	12
1.1.2	Series circuits	12
1.1.3	Parallel circuits	12
1.2	Integrated circuits	12
1.3	Circuit boards	12
1.4	Inside actual electronic devices	12
2	Describing sources: AC / DC	13
3	Transients	14
4	The bare minimum of practical tips	15
4.1	Measuring with a multimeter	15
4.2	Mains power	15
II	Analog electronics	16
5	Ideal linear components	17
5.1	Voltage and current sources	17
5.2	Resistors	17
5.2.1	Ohm's law	17
5.2.2	Potentiometers	17
5.2.3	Resistors in circuits	17
5.2.3.1	Resistors in parallel	17
5.2.3.2	Resistors in series	17
	Voltage divider	17
5.3	Capacitors	17
5.3.1	Capacitors in circuits	17
5.3.1.1	Capacitors in parallel	17
5.3.1.2	Capacitors in series	17

	Capacitive divider	17
5.3.2	Capacitive reactance	18
5.3.3	Quality factor	18
5.4	Inductors	18
5.4.1	Inductors in circuits	18
	5.4.1.1 Inductors in parallel	18
	5.4.1.2 Inductors in series	18
5.4.2	Inductive reactance	18
5.4.3	Quality factor	18
5.4.4	Unwanted coupling: spikes	18
5.5	Transformers	18
5.6	Crystals and resonators	18
6	Analysis of linear circuits	19
6.1	Kirchhoff's laws	19
	6.1.1 Voltage law <i>or</i> loop rule	19
	6.1.2 Current law <i>or</i> junction rule	19
	6.1.3 Result: systems of linear equations	19
6.2	Superposition principle	19
6.3	Thévenin's and Norton's theorems	19
	6.3.1 Thévenin's theorem	19
	6.3.2 Norton's theorem	19
	6.3.3 Nodal analysis	19
	6.3.4 Mesh analysis	19
6.4	Power in AC circuits	19
	6.4.1 Power factor	19
6.5	Circuits with sinusoidal sources	19
6.6	Circuits with periodic non-sinusoidal sources	19
7	Elements of circuits	20
7.1	Resonance	20
	7.1.1 Series-resonant circuits	20
	7.1.1.1 LC	20
	7.1.1.2 LRC	20
	7.1.1.3 Bandwidth	20
	7.1.1.4 Quality factor	20
	7.1.2 Parallel-resonant (antiresonant) circuits	20
	7.1.2.1 LC	21
	7.1.2.2 LRC	21
	7.1.2.3 Bandwidth	21
	7.1.2.4 Quality factor	21
7.2	Input and output impedance	21
7.3	Filters	21
	7.3.1 Passive filter	21
	7.3.1.1 Low-pass filters	21
	7.3.1.2 High-pass filters	21
	7.3.1.3 Bandpass filters	21
	7.3.1.4 Notch filters	21
	7.3.1.5 Speaker crossover network	21

7.3.2	Active filters	21
7.3.2.1	Low-pass RC active audio filter	21
7.3.2.2	High-pass RC active audio filter	21
7.4	RC ripple filter	21
7.5	Attenuators	21
7.6	Coupling and DC blocking	21
7.7	Bypassing	21
7.8	Arc suppression	21
7.9	Switching regulators	21
8	Non-ideal components and models	22
8.1	Wires	22
8.1.1	Non-ideal behaviour	22
8.1.1.1	Wire resistance	22
8.1.1.2	Wire inductance	22
8.1.1.3	Skin effect	22
8.1.1.4	Cable impedance	22
	Inductance	22
	Capacitance	22
	Impedance matching	22
	Circuit solutions	22
8.1.2	Forms of wire	22
8.1.2.1	Solid core wire	22
8.1.2.2	Stranded wire	23
8.1.2.3	Braided wire	23
8.1.3	Kinds of wires	23
8.1.4	Kinds of cables	23
8.1.5	Kinds of connectors	23
8.1.6	Symbols	23
8.1.6.1	Wiring	23
8.1.6.2	Connectors	23
8.2	Switches	23
8.2.1	Kinds of switch	24
8.2.2	Relays	24
8.2.2.1	Kinds of relays	24
8.2.2.2	Relay driver circuit	24
8.2.3	Symbols for switches	24
8.3	Resistors	24
8.3.1	Realistic model	24
8.3.2	Characteristics of real capacitors	24
8.3.2.1	Tolerance	24
8.3.2.2	Power rating	24
8.3.2.3	Temperature coefficient of resistance	24
8.3.3	Resistor labels	24
8.3.4	Types of resistors	24
8.3.5	Variable resistors	24
8.3.5.1	Resistance taper	24
8.3.5.2	Types	24
8.4	Capacitors	24

8.4.1	Realistic model	24
8.4.2	Characteristics of real capacitors	25
8.4.2.1	Dissipation factor	25
8.4.2.2	Insulation resistance	25
8.4.2.3	Dissipation factor or tangent delta ($\tan \delta$)	25
8.4.3	Types of capacitors	25
8.5	Inductors	25
8.5.1	Geometries of inductor configurations	25
8.5.1.1	Simple coil	25
8.5.1.2	Multilayer coil	25
8.5.1.3	Spiral coil	25
8.5.1.4	Toroidal coil	25
8.5.2	Realistic model	25
8.5.3	Inductor specifications	25
8.5.4	Types of inductors	25
8.5.5	Reading inductor labels	25
8.5.5.1	5-band inductor codes	25
8.5.5.2	4-band inductor codes	25
8.5.5.3	SMD inductance codes	25
8.6	Transformers	25
8.7	Batteries	25
8.7.1	Battery capacity	26
8.7.2	Internal resistance	26
8.7.3	Combining batteries	26
8.7.4	Battery packages	26
8.7.5	Primary batteries	26
8.7.6	Secondary batteries	26
8.8	Ground	26
8.9	Power supplies	26
8.10	Fuses and circuit breakers	26
9	Active components	27
9.1	Semiconductor physics	27
9.2	Diodes	27
9.2.1	Static behaviour: a simple model	27
9.2.2	Dynamic, or transient, behaviour	27
9.2.2.1	Depletion-region capacitance	27
	Abrupt junction	27
	Linearly graded junction	28
	Large-signal depletion-region capacitance.	28
9.2.2.2	Excess minority carrier charge	28
9.2.3	Secondary effect: a more accurate model	28
9.2.3.1	Breakdown	28
	Avalanche breakdown.	28
	Zener breakdown.	28
9.2.3.2	Emission coefficient	28
9.3	Thyristors and triacs	28
9.4	Bipolar transistors (BJTs)	28
9.5	Junction field effect transistors (FETs)	28

9.6	Metal oxide field effect transistors (MOSFETs)	28
9.6.1	Static behaviour	28
9.6.1.1	Cut-off region	28
9.6.1.2	Ohmic region	29
9.6.1.3	Saturation region	29
9.6.2	Some secondary effects	29
9.6.2.1	Channel length modulation	29
9.6.2.2	Velocity saturation	30
	A simpler model	30
9.6.2.3	Threshold variations	30
9.6.2.4	Hot-carrier effects	30
9.6.2.5	CMOS latchup	30
9.6.3	Dynamic behaviour	30
9.6.3.1	Capacitive device model	30
	MOS structure capacitances	30
	Channel capacitances	30
	Junction capacitances	30
9.6.3.2	Source-drain resistance	30
9.6.4	Comparison NMOS and PMOS	30
9.6.5	SPICE models	30
9.6.6	Process variations	30
9.6.7	Technology scaling	30
9.7	Insulated-gate bipolar transistors (IGBTs)	30
10	Analogue integrated circuits	31
10.1	The ideal op-amp	31
10.2	The practical op-amp	31
10.3	Comparators	31
10.4	Voltage references	31
11	Classic circuits	32
11.1	Rectifiers	32
11.2	Switching regulators	32
11.2.1	Buck converter	32
11.2.2	Boost converter	32
11.2.3	Buck-boost converter	32
11.3	Oscillators	32
11.3.1	Simple relaxation oscillator	32
11.3.2	Op-amp oscillator	32
11.3.3	Colpits oscillator	32
11.3.4	Hartley oscillator	32
11.4	Radio circuits	32
11.4.1	Short-wave receiver	32
11.4.2	RF oscillator / transmitter	32
12	Filters	33
13	Oscillators and timers	34
14	Voltage regulation and power conversion	35

15 PCB design tips	36
III Digital electronics	37
16 Introduction	38
16.1 Manufacturing CMOS integrated circuits	38
16.2 Design rules	38
16.3 Packaging integrated circuits	38
17 Boolean algebra and gates	39
17.1 Algebraic properties	39
17.2 Axiomatic definition	39
17.3 Basic theorems	39
17.4 Canonical and standard forms	39
17.5 Simplification of Boolean functions	39
17.5.1 Karnaugh maps	39
17.5.2 Don't-care conditions	39
17.5.3 The tabulation method	39
17.6 Time evolution and sequential logic	39
18 Some ideal digital components	40
18.1 Combinational logic components	40
18.1.1 Carry-ripple adders	40
18.1.2 Carry-look-ahead adders	40
18.1.3 Adders and subtractors	40
18.1.4 Logic unit and arithmetic-logic unit	40
18.1.5 Decoders	40
18.1.6 Selectors	40
18.1.7 Buses	40
18.1.8 Priority encoders	40
18.1.9 Magnitude comparators	40
18.1.10 Shifters and rotators	40
18.1.11 Read-Only memories	40
18.1.12 Programmable logic arrays	40
18.2 Sequential logic components	40
18.2.1 Latches	40
18.2.1.1 SR-latch	40
18.2.1.2 Gated SR-latch	40
18.2.1.3 Gated D-latch	40
18.2.2 Flip-flops	40
18.2.3 Analysis of sequential logic	41
18.3 Storage components	41
18.3.1 Registers	41
18.3.1.1 Shift registers	41
18.3.2 Counters	41
18.3.2.1 BCD counter	41
18.3.2.2 Asynchronous counter	41
18.3.3 Random-access memories (RAMs)	41

19 Designing digital integrated circuits	42
19.1 Design parameters	42
19.1.1 Cost	42
19.1.2 Performance	43
19.1.2.1 Ring oscillators	43
19.1.3 Functionality and robustness	43
Noise margins	43
Noise immunity	43
Regenerative property.	43
Directivity.	43
Fan-out	43
Fan-in	44
19.1.4 Power and energy consumption	44
19.2 Design methodologies	44
19.2.1 Custom circuit design	44
19.2.2 Cell-based	44
19.2.2.1 Standard cell	44
19.2.2.2 Compiled cell	44
19.2.2.3 Macro cells	44
19.2.3 Array-based	44
19.2.3.1 Prediffused (or mask-programmable) arrays	44
19.2.3.2 Prewired arrays (FPGAs)	44
19.3 Coping with interconnect	44
19.4 Timing issues	44
19.4.1 Timing classification	44
20 Designing gates and components	45
20.1 Transistor-transistor logic (TTL)	45
20.2 CMOS technology	45
20.2.1 The CMOS inverter	45
20.2.2 Combinational logic in CMOS	45
20.2.3 Sequential logic in CMOS	45
21 Processors and microcontrollers	46
IV Electric devices	47
22 Motors and actuators	48
23 Audioelectronics	49
24 Optoelectronics	50
25 Radio engineering	51

V	Multiphase systems	52
VI	General design practices	53
25.1	Precision and low noise	54
VII	Simulation	55
25.2	Spice	56
25.3	Verilog	56
VIII	Tools and accessories	57
26	Hardware	58
26.1	Screws	58
27	Devices	59
27.1	Power supplies	59
27.1.1	Bench power supply	59
27.2	Oscilloscopes	59
27.2.1	Probes	59
27.2.1.1	Isolation	59
27.2.1.2	Types	60
27.2.2	Controls	60
A	Symbols and constants	61
B	Formula reference	62
C	Bibliography	63
	tie inputs high / low: good practice	
	capacitors at input / output to reduce noise	
	timing with RC and Schmidt trigger	

Chapter 0

Preface

Part I

Introducing some basic ideas

heat conduction / thermal resistance
ground
decibels

Chapter 1

Different types of circuits

1.1 Basic circuits

1.1.1 Wires

1.1.2 Series circuits

1.1.3 Parallel circuits

1.2 Integrated circuits

1.3 Circuit boards

1.4 Inside actual electronic devices

Chapter 2

Describing sources: AC / DC

RMS / peak

Chapter 3

Transients

Chapter 4

The bare minimum of practical tips

4.1 Measuring with a multimeter

4.2 Mains power

Part II

Analog electronics

Chapter 5

Ideal linear components

5.1 Voltage and current sources

5.2 Resistors

5.2.1 Ohm's law

5.2.2 Potentiometers

5.2.3 Resistors in circuits

5.2.3.1 Resistors in parallel

5.2.3.2 Resistors in series

Voltage divider 10 percent rule (of total load current when multiload)

5.3 Capacitors

5.3.1 Capacitors in circuits

5.3.1.1 Capacitors in parallel

5.3.1.2 Capacitors in series

Capacitive divider

5.3.2 Capacitive reactance

5.3.3 Quality factor

5.4 Inductors

5.4.1 Inductors in circuits

5.4.1.1 Inductors in parallel

5.4.1.2 Inductors in series

5.4.2 Inductive reactance

5.4.3 Quality factor

5.4.4 Unwanted coupling: spikes

5.5 Transformers

5.6 Crystals and resonators

Chapter 6

Analysis of linear circuits

Miller effect??

6.1 Kirchhoff's laws

6.1.1 Voltage law *or* loop rule

6.1.2 Current law *or* junction rule

6.1.3 Result: systems of linear equations

6.2 Superposition principle

6.3 Thévenin's and Norton's theorems

6.3.1 Thévenin's theorem

6.3.2 Norton's theorem

6.3.3 Nodal analysis

6.3.4 Mesh analysis

6.4 Power in AC circuits

Apparent power, real power, reactive power

6.4.1 Power factor

6.5 Circuits with sinusoidal sources

6.6 Circuits with periodic non-sinusoidal sources

Chapter 7

Elements of circuits

7.1 Resonance

7.1.1 Series-resonant circuits

7.1.1.1 LC

7.1.1.2 LRC

7.1.1.3 Bandwidth

7.1.1.4 Quality factor

7.1.2 Parallel-resonant (antiresonant) circuits

More common

7.1.2.1 LC

7.1.2.2 LRC

7.1.2.3 Bandwidth

7.1.2.4 Quality factor

7.2 Input and output impedance

7.3 Filters

7.3.1 Passive filter

7.3.1.1 Low-pass filters

7.3.1.2 High-pass filters

7.3.1.3 Bandpass filters

7.3.1.4 Notch filters

7.3.1.5 Speaker crossover network

7.3.2 Active filters

7.3.2.1 Low-pass RC active audio filter

7.3.2.2 High-pass RC active audio filter

7.4 RC ripple filter

7.5 Attenuators

7.6 Coupling and DC blocking

7.7 Bypassing

7.8 Arc suppression

7.9 Switching regulators

Chapter 8

Non-ideal components and models

8.1 Wires

- Not breaking
- Not overheating
- Clean signal

Wire vs cable

8.1.1 Non-ideal behaviour

8.1.1.1 Wire resistance

8.1.1.2 Wire inductance

8.1.1.3 Skin effect

8.1.1.4 Cable impedance

Inductance

Capacitance

Impedance matching

Circuit solutions

8.1.2 Forms of wire

8.1.2.1 Solid core wire

TODO table of wire gauges.

8.1.2.2 Stranded wire

8.1.2.3 Braided wire

8.1.3 Kinds of wires

- Pretinned solid bus wire
- Speaker wire
- Magnet wire

8.1.4 Kinds of cables

- Paired cable
- Twisted pair
- Unbalanced coaxial
- Dual coaxial
- Balanced coaxial
- Shielded twin lead
- Ribbon
- Multiple conductor
- Fiberoptic
- 300Ω

8.1.5 Kinds of connectors

8.1.6 Symbols

8.1.6.1 Wiring

8.1.6.2 Connectors

8.2 Switches

- Wear: depends on speed (arcing)

8.2.1 Kinds of switch

8.2.2 Relays

8.2.2.1 Kinds of relays

8.2.2.2 Relay driver circuit

8.2.3 Symbols for switches

8.3 Resistors

8.3.1 Realistic model

8.3.2 Characteristics of real capacitors

8.3.2.1 Tolerance

8.3.2.2 Power rating

power rating twice maximum

8.3.2.3 Temperature coefficient of resistance

8.3.3 Resistor labels

8.3.4 Types of resistors

Groups:

- General purpose
- Precision
- Semiprecision
- Power resistors

8.3.5 Variable resistors

Rheostats, potentiometers, trimmers

8.3.5.1 Resistance taper

8.3.5.2 Types

8.4 Capacitors

8.4.1 Realistic model

Leakage, equivalent series resistance, equivalent series inductance, dielectric absorption

8.4.2 Characteristics of real capacitors

8.4.2.1 Dissipation factor

8.4.2.2 Insulation resistance

8.4.2.3 Dissipation factor or tangent delta ($\tan \delta$)

8.4.3 Types of capacitors

8.5 Inductors

8.5.1 Geometries of inductor configurations

8.5.1.1 Simple coil

8.5.1.2 Multilayer coil

8.5.1.3 Spiral coil

8.5.1.4 Toroidal coil

8.5.2 Realistic model

8.5.3 Inductor specifications

8.5.4 Types of inductors

8.5.5 Reading inductor labels

8.5.5.1 5-band inductor codes

8.5.5.2 4-band inductor codes

8.5.5.3 SMD inductance codes

8.6 Transformers

8.7 Batteries

- Size
- Power
- Voltage
- Current capacity
- Rechargeability

- 8.7.1 Battery capacity**
- 8.7.2 Internal resistance**
- 8.7.3 Combining batteries**
- 8.7.4 Battery packages**
- 8.7.5 Primary batteries**
- 8.7.6 Secondary batteries**

8.8 Ground

Symbols for ground

Ground loops (and single-point ground; ground bus)
separate digital and analog grounds

8.9 Power supplies

8.10 Fuses and circuit breakers

Chapter 9

Active components

9.1 Semiconductor physics

9.2 Diodes

There is a built-in potential across the junction:

$$\phi_0 = \phi_T \ln \left[\frac{N_A N_D}{n_i^2} \right]$$

where ϕ_T is the thermal voltage

$$\phi_T = \frac{kT}{q} = 26 \text{ mV} \quad \text{at room temperature.}$$

9.2.1 Static behaviour: a simple model

Ideal diode equation

$$I_D = I_S (e^{V_D/\phi_T} - 1)$$

9.2.2 Dynamic, or transient, behaviour

9.2.2.1 Depletion-region capacitance

Abrupt junction

$$Q_j = A_D \sqrt{\left(2\epsilon_{si} q \frac{N_A N_D}{N_A + N_D} \right) (\phi_0 - V_D)}$$

Width

$$W_j = W_2 - W_1 = A_D \sqrt{\left(\frac{2\epsilon_{si}}{q} \frac{N_A + N_D}{N_A N_D} \right) (\phi_0 - V_D)}$$

$$\frac{W_2}{-W_1} = \frac{N_A}{N_D}$$

$$E_j = A_D \sqrt{\left(\frac{2q}{\epsilon_{si}} \frac{N_A N_D}{N_A + N_D} \right) (\phi_0 - V_D)}$$

$$C_j = \frac{dQ_j}{dV_D} = A_D \sqrt{\left(\frac{\epsilon_{si} q}{2} \frac{N_A N_D}{N_A + N_D} \right) (\phi_0 - V_D)^{-1}}$$

$$= \frac{C_{j0}}{\sqrt{1 - V_D/\phi_0}}$$

Linearly graded junction

$$C_j = \frac{C_{j0}}{(1 - V_D/\phi_0)^m}$$

where m is the grading coefficient.

Large-signal depletion-region capacitance.

9.2.2.2 Excess minority carrier charge

9.2.3 Secondary effect: a more accurate model

9.2.3.1 Breakdown

Avalanche breakdown. This occurs when carriers crossing the depletion-region are accelerated enough to create electron-hole pairs when they collide with silicon atoms.

Zener breakdown.

9.2.3.2 Emission coefficient

9.3 Thyristors and triacs

9.4 Bipolar transistors (BJTs)

9.5 Junction field effect transistors (FETs)

9.6 Metal oxide field effect transistors (MOSFETs)

Advantages:

- Few parasitic effects
- Simple planar manufacturing process

9.6.1 Static behaviour

9.6.1.1 Cut-off region

If we apply a positive voltage to the gate, a depletion region forms

$$W_d = \sqrt{\frac{2\epsilon_{si}\phi}{qN_A}}$$

$$Q_d = \sqrt{2qN_A\epsilon_{si}\phi}$$

When the voltage equals twice the Fermi potential

$$\phi_F = \phi_T \ln \left(\frac{N_A}{n_i} \right) \approx -0.3 \text{ V}$$

strong inversion occurs. The depletion layer no longer grows, but a layer of electrons forms.

$$Q_B = \sqrt{2qN_A\epsilon_{si}(|-2\phi_F + V_{SB}|)}$$

We determine the threshold voltage empirically and use

$$V_T = V_{T0} + \gamma(\sqrt{|V_{SB} - 2\phi_F|} - \sqrt{|2\phi_F|})$$

with γ the body effect coefficient.

9.6.1.2 Ohmic region

Charge per unit area

$$Q_i(x) = -C_{ox}[V_{GS} - V(x) - V_T]$$

Current flow:

$$I_D = -v_n(x)Q_i(x)W$$

where the electron velocity is related to the mobility μ_n

$$v_n = -\mu_n \xi(x) = \mu_n \frac{dV}{dx}$$

Combining we get

$$I_D dx = \mu_n C_{ox} W (V_{GS} - V - V_T) dV$$

Integrating over length of channel L :

$$\begin{aligned} I_D &= k'_n \frac{W}{L} \left[(V_{GS} - V_T)V_{DS} - \frac{V_{DS}^2}{2} \right] \\ &= k_n \left[(V_{GS} - V_T)V_{DS} - \frac{V_{DS}^2}{2} \right] \end{aligned}$$

For small V_{DS} we can ignore the quadratic term. Then the relation between V_{DS} and I_D is linear.

9.6.1.3 Saturation region

When

$$\begin{aligned} V_{GS} - V_{DS} &\leq V_T \\ I_D &= \frac{k'_n}{2} \frac{W}{L} (V_{GS} - V_T)^2 \end{aligned}$$

9.6.2 Some secondary effects

9.6.2.1 Channel length modulation

$$I_D = I'_D(1 + \lambda V_{DS})$$

9.6.2.2 Velocity saturation

$$v = \begin{cases} \frac{\mu_n \xi}{1 + \xi/\xi_c} & (\xi \leq \xi_c) \\ v_{sat} & (\xi \geq \xi_c) \end{cases}$$

More time in saturation for short devices.

I_{DSAT} depends linearly on $V_G S$.

A simpler model

9.6.2.3 Threshold variations

9.6.2.4 Hot-carrier effects

9.6.2.5 CMOS latchup

9.6.3 Dynamic behaviour

9.6.3.1 Capacitive device model

MOS structure capacitances

Channel capacitances

Junction capacitances

9.6.3.2 Source-drain resistance

9.6.4 Comparison NMOS and PMOS

- Velocity saturation less pronounced in PMOS.

9.6.5 SPICE models

9.6.6 Process variations

9.6.7 Technology scaling

9.7 Insulated-gate bipolar transistors (IGBTs)

Chapter 10

Analogue integrated circuits

large analog ICs not very abstractable

10.1 The ideal op-amp

10.2 The practical op-amp

10.3 Comparators

10.4 Voltage references

Chapter 11

Classic circuits

11.1 Rectifiers

11.2 Switching regulators

11.2.1 Buck converter

11.2.2 Boost converter

11.2.3 Buck-boost converter

11.3 Oscillators

11.3.1 Simple relaxation oscillator

11.3.2 Op-amp oscillator

11.3.3 Colpits oscillator

11.3.4 Hartley oscillator

11.4 Radio circuits

11.4.1 Short-wave receiver

11.4.2 RF oscillator / transmitter

Chapter 12

Filters

Chapter 13

Oscillators and timers

Chapter 14

Voltage regulation and power conversion

Chapter 15

PCB design tips

Part III

Digital electronics

Chapter 16

Introduction

16.1 Manufacturing CMOS integrated circuits

16.2 Design rules

16.3 Packaging integrated circuits

Chapter 17

Boolean algebra and gates

17.1 Algebraic properties

17.2 Axiomatic definition

17.3 Basic theorems

17.4 Canonical and standard forms

17.5 Simplification of Boolean functions

17.5.1 Karnaugh maps

17.5.2 Don't-care conditions

17.5.3 The tabulation method

17.6 Time evolution and sequential logic

Chapter 18

Some ideal digital components

18.1 Combinational logic components

18.1.1 Carry-ripple adders

18.1.2 Carry-look-ahead adders

18.1.3 Adders and subtractors

18.1.4 Logic unit and arithmetic-logic unit

18.1.5 Decoders

18.1.6 Selectors

18.1.7 Buses

18.1.8 Priority encoders

18.1.9 Magnitude comparators

18.1.10 Shifters and rotators

18.1.11 Read-Only memories

18.1.12 Programmable logic arrays

18.2 Sequential logic components

18.2.1 Latches

18.2.1.1 SR-latch

18.2.1.2 Gated SR-latch

18.2.1.3 Gated D-latch

18.2.2 Flip-flops

Flip-flop types

18.2.3 Analysis of sequential logic

18.3 Storage components

18.3.1 Registers

18.3.1.1 Shift registers

18.3.2 Counters

18.3.2.1 BCD counter

18.3.2.2 Asynchronous counter

18.3.3 Random-access memories (RAMs)

Chapter 19

Designing digital integrated circuits

Divide-and-conquer: hierarchy, but clocks and power defy hierarchy - global and external issues
die, wafer, masks

19.1 Design parameters

19.1.1 Cost

The cost of an integrated circuit can be split into fixed costs, such as the cost of designing the IC, indirect costs for general company overhead and variable costs which is the cost directly attributable to the manufactured product:

$$\text{cost per IC} = \text{variable cost per IC} + \left(\frac{\text{fixed cost} + \text{indirect cost}}{\text{volume}} \right)$$

The fixed cost is strongly dependent on complexity and its impact is much more pronounced for small-volume products.

The variable cost is made up of the cost of the die plus the cost of testing and packaging, where the cost of the die is given by

$$\text{cost of die} = \frac{\text{cost of wafer}}{\text{dies per wafer} \times \text{die yield}}.$$

The die yield gives the proportion of dies that do not have a defect and, assuming defects are randomly distributed, can be expressed as

$$\text{die yield} = \left(1 + \frac{\text{defects per unit area} \times \text{die area}}{\alpha} \right)^{-\alpha}$$

where α is a parameter that depends on the complexity of the manufacturing process and is roughly proportional to the number of masks. For modern CMOS processes $\alpha \approx 3$. One can expect about 0.5 to 1 defects per cm^2 , but this depends strongly on the maturity of the process. Using $\alpha = 3$, we see that

$$\text{cost of die} \sim (\text{die area})^4$$

so the die area is a prime metric for the cost.

19.1.2 Performance

Obviously we want our ICs to be as fast as possible.

For processors the speed depends on both the architecture of the processor (e.g. how many commands it can execute in parallel) and its clock speed.

For individual gates the performance is determined by the **propagation delay** t_p which is how quickly the output responds to changes in input. In other words it is the delay experienced by a signal traveling through the gate. This delay actually also depends on the input signal. In particular its slope (see figure TODO). For that reason we introduce the quantities t_r and t_f which are the rise and fall times.

19.1.2.1 Ring oscillators

The de facto way to measure delays for a given circuit technology is with a ring oscillator, which is an odd number (usually at least five are needed) of inverters put back-to-back in a loop. This configuration has no stable state and thus will oscillate. The frequency of the oscillation is proportional to the propagation delay.

This method is primarily useful to compare different technologies, not to determine actual values for t_p . The situation is fairly ideal with minimal load. In actual circuits t_p may be expected to be 50 to 100 times slower.

19.1.3 Functionality and robustness

In real life nothing is perfect, but the output of an integrated circuits must be within an acceptable range, even if the conditions it is deployed in are not ideal.

A good design accounts for variations in the manufacturing process and must also be able to deal with *noise*, which is unexpected variation in the signal. Noise can also easily be generated within the IC if the input is rapidly changing for example. A good design will not introduce too much noise itself.

Noise margins are the ranges that the input voltage has to be in to be interpreted as either low or high. Ideally these are as large as possible.

Noise immunity refers to the ability to function correctly in the presence of noise. Many digital circuits with low noise margins have very good noise immunity because they reject the noise.

Regenerative property. If every gate adds a bit of noise, the signal will eventually be lost. Thus an important property of gates is the ability to bring back the signal to nominal levels after a disturbance.

Directivity. We in general want gates to be *unidirectional*: changes in output should not impact the input. In practice there will always be some capacitive coupling for instance.

Fan-out refers to the number of gates attached to the output. With large fan-out, the added load can reduce performance. For this reason library components often specify a maximum fan-out.

The added load can also affect the logic output levels. In order to minimise this effect, the input resistance is made as large as possible while keeping the output resistance small.

Fan-in is the number of inputs. More inputs means more complexity.

19.1.4 Power and energy consumption

Power considerations are very important. This was the main limiting factor for vacuum tube and bipolar technologies. It is also the reason CMOS is much more popular than pure NMOS (TODO ?), although now even CMOS is reaching its limits in this regard.

Power and energy consumption can be measured with different metrics. Obviously we can measure peak and average power dissipation, P_{peak} and P_{av} . It is also useful to decompose power consumption into *static* and *dynamic* components. The higher the number of switching events, the higher the dynamic power consumption.

The propagation delay and power consumption of a gate are related: the propagation delay is mostly determined by the speed at which a given amount of energy can be stored in the gate capacitors. For a given technology and gate topology, the product of the power consumption and propagation delay is generally a constant, called the power-delay product (PDP). This is simply the energy consumed per switching event and is a good quality measure for a switching device.

19.2 Design methodologies

19.2.1 Custom circuit design

19.2.2 Cell-based

19.2.2.1 Standard cell

19.2.2.2 Compiled cell

19.2.2.3 Macro cells

19.2.3 Array-based

19.2.3.1 Prediffused (or mask-programmable) arrays

19.2.3.2 Prewired arrays (FPGAs)

19.3 Coping with interconnect

19.4 Timing issues

19.4.1 Timing classification

Chapter 20

Designing gates and components

20.1 Transistor-transistor logic (TTL)

20.2 CMOS technology

20.2.1 The CMOS inverter

20.2.2 Combinational logic in CMOS

20.2.3 Sequential logic in CMOS

Chapter 21

Processors and microcontrollers

Intel 4004 in 1972 and 8080 in 1974 (IBM computers? Instruction set)

Part IV

Electric devices

Chapter 22

Motors and actuators

Chapter 23

Audioelectronics

Chapter 24

Optoelectronics

Chapter 25

Radio engineering

Part V

Multiphase systems

Part VI

General design practices

25.1 Precision and low noise

Part VII

Simulation

25.2 Spice

25.3 Verilog

Part VIII

Tools and accessories

Chapter 26

Hardware

26.1 Screws

Chapter 27

Devices

27.1 Power supplies

27.1.1 Bench power supply

Output: three terminals: positive, negative and ground. Ground should be isolated from other terminals.

27.2 Oscilloscopes

The main function of an oscilloscope is the measure voltage in function of time. Time is on the horizontal axis.

If the signal is periodic, it is easiest if one point in the cycle is fixed on the horizontal axis. This is achieved with triggering: every time the signal does something specific (the trigger event), the plot is shifted so that time is at a designated point on the screen. Typically a trigger event is when the signal passes a certain threshold and is either rising or falling.

27.2.1 Probes

Usually BNC connector on one end and other end has measuring tip and alligator clip for reference.

27.2.1.1 Isolation

It is important that the circuit being measured is completely isolated from the oscilloscope. If this is not the case and the ground clip is connected to a part of the circuit that is not ground, then this will complete a low resistance path to ground, causing much current to flow.

Usually oscilloscopes probes are connected to the ground of the grid. So the circuit being tested should be isolated from the grid! It is done this way round for a couple of reasons: as soon as the scope is connected to something else, e.g. to a computer via USB, then it is no longer floating. Also floating a scope may leave it with charge that will discharge through the next user.

If the circuit being measured cannot be isolated, then differential probes can be used. There are also devices for galvanically isolating USB connections. Remember that a circuit connected by USB is not isolated!

27.2.1.2 Types

There are three basic types: 1X, 10X and 100X.

27.2.2 Controls

Most oscilloscopes have the following controls:

- Moving vertical position up and down.
- Change scale of time and voltage axis. This is often labelled as seconds / division and volts / division. Some scopes have a button or a sensing device (Tektronix) to know whether the probe is 1X or 10X. All this does is change the label on the voltage axis.
- Coupling: DC, AC and ground. DC shows the signal as is, AC translates the signal vertically such that the average is zero and ground disconnects the signal.
- Setting trigger type.
- Autoset tries to find settings that show something of the signal. Very useful if you don't know why a signal is not showing up.

Appendix A

Symbols and constants

Appendix B

Formula reference

Appendix C

Bibliography

The Art of Electronics

The circuit designers handbook, williams

Digital integrated circuits, a design perspective; Rabaey, Chandrakasan and Nikolic

Electrische energie; Ronnie Belmans, Geert Deconinck, Johan Driesen

1. Analog circuits:

- <https://www.allaboutcircuits.com/textbook/>